

EECS 16B Midterm 1 Review Session

Presented by Bryan Ngo, Rohin Tangirala (HKN)

Disclaimer

This is an unofficial review session and HKN is not affiliated with this course. Although some of the presenters may be course staff, the material covered in the review session may not be an accurate representation of the topics covered in and difficulty of the exam.

Slides are also posted at @1046 on Piazza.


This is licensed under the Creative Commons CC BY-SA: feel free to share and edit, as long as you credit us and keep the license. For more information, visit <https://creativecommons.org/licenses/by-sa/4.0/>

HKN Drop-In Tutoring

- HKN has office hours Monday, Wednesday, and Friday from **1 PM - 3 PM** and **8 PM - 10 PM** on hkn.mu/ohqueue
- The schedule of tutors can be found at hkn.mu/tutor

CMOS Transistors and Logic

Transistors

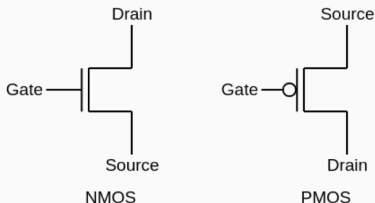

Two varieties of MOSFETs: P-type and N-type


Any MOSFET has a characteristic threshold voltage V_{th}

NMOS "turns on" (connects drain to source) when $V_{GS} > V_{th}$

PMOS turns on when $V_{GS} < V_{th}$

NMOS Logic

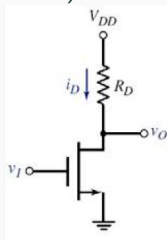We can build an inverter (a circuit that flips a 1 to a 0 and vice versa) with a single N-type MOSFET!




What is v_O when $v_I > V_{th}$? When $v_I < V_{th}$?

Key disadvantage: what is the power dissipated when $v_I > V_{th}$?


How can we rectify this?

CMOS Logic

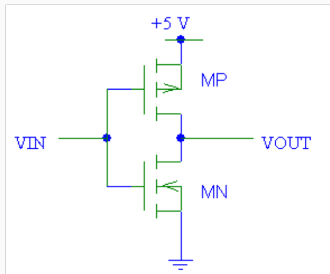

Now, we have the same logical function as the NMOS inverter, but we're using more transistors and much less power is dissipated. Why?

CMOS Logic

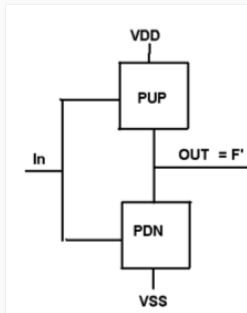

This is broadly called Complementary Metal Oxide Semiconductor (CMOS) logic, using a Pull-Up Network of P-type and a Pull-Down Network of N-type MOSFETs.

Now we can build circuits that perform logical functions out of MOSFETs!

True or False:

1. Power (in the EE16B model) is dissipated in a CMOS circuit only when there is switching
2. NMOS devices turn on with a large V_{GS} and off with low V_{GS}
3. For a given choice of inputs in a CMOS inverter circuit, we can create a low resistance path from ground to high voltage

True or False:

1. Power (in the EE16B model) is dissipated in a CMOS circuit only when there is switching

True

2. NMOS devices turn on with a large V_{GS} and off with low V_{GS}
3. For a given choice of inputs in a CMOS inverter circuit, we can create a low resistance path from ground to high voltage

True or False:

1. Power (in the EE16B model) is dissipated in a CMOS circuit only when there is switching

True

2. NMOS devices turn on with a large V_{GS} and off with low V_{GS}

True

3. For a given choice of inputs in a CMOS inverter circuit, we can create a low resistance path from ground to high voltage

True or False:

1. Power (in the EE16B model) is dissipated in a CMOS circuit only when there is switching

True

2. NMOS devices turn on with a large V_{GS} and off with low V_{GS}

True

3. For a given choice of inputs in a CMOS inverter circuit, we can create a low resistance path from ground to high voltage


False

RC Circuits

RC Circuits

The capacitor and resistor in a NOT circuit form the most basic RC circuit:

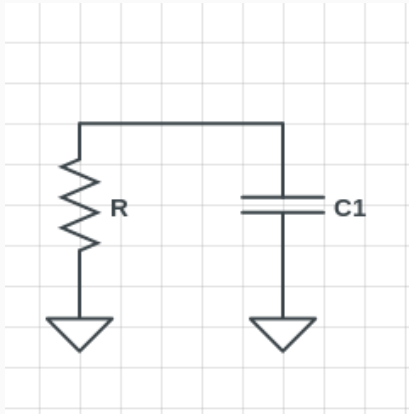
Write down a differential equation describing the circuit below:



RC Circuits

The capacitor and resistor in a NOT circuit form the most basic RC circuit:

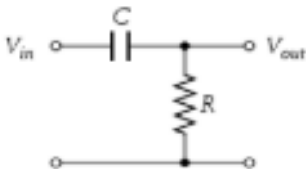Write down a differential equation describing the circuit below:



Solving the RC differential Equation

We have a differential equation describing V_{out} in terms of V_c .

$$\frac{dV_c}{dt} = -\frac{1}{RC} V_c$$

How do we actually solve it?

Solving the RC differential Equation

We have a differential equation describing V_{out} in terms of V_c .

$$\frac{dV_c}{dt} = -\frac{1}{RC} V_c$$

How do we actually solve it?

Think of the differential operation as a linear operator that scales V_c , since V_c is one of its eigenfunctions:

$$\left[\frac{d}{dt}\right] V_c = \lambda V_c$$

Solving the RC differential Equation

Which are the eigenfunctions of differentiation?

Solving the RC differential Equation

Which are the eigenfunctions of differentiation?

$$Ae^{\lambda t}$$

Solving the RC differential Equation

Which are the eigenfunctions of differentiation?

$$Ae^{\lambda t}$$


$$\frac{dV_c}{dt} = -\frac{1}{RC} V_c$$

The solution to our first order differential equations is therefore:

$$V_c(t) = V_c(0)e^{\frac{-1}{RC}t}$$

RC Differential Equation: Non-homogenous case

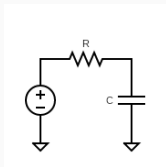How do you solve a RC circuit with a voltage source?



Applying KCL at the top right node, along with Ohm's law and the capacitor relationship, we get:

$$\frac{dV_c}{dt} = \frac{1}{RC}(V_s - V_c)$$

We can't easily solve this equation, so we change variables to

$$x = V_c - V_s$$

RC Differential Equation: Non-homogenous case

Now, we have $\frac{dx}{dt} = -\frac{x}{RC}$

We already know how to solve this differential equation, and we get

$$x(t) = x_0 e^{-\frac{t}{RC}}$$

Finally, change back to the original variables by substituting $V_c - V_s$ for x

$$V_c(t) = V_c(0)e^{-\frac{t}{RC}} + V_s(1 - e^{-\frac{t}{RC}})$$

Change of Basis

Change of Basis

In the standard basis, we write vectors as a linear combination of the standard basis vectors.

$$\vec{x} = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = x_1 \begin{bmatrix} 1 \\ 0 \end{bmatrix} + x_2 \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

Likewise, we can write our x vector as a linear combination of some other basis vectors. For example, if our V -basis has basis vectors \vec{v}_1 and \vec{v}_2 :

$$\vec{x} = \tilde{x}_1 \cdot \vec{v}_1 + \tilde{x}_2 \cdot \vec{v}_2 = V\tilde{x}$$

We can go from the V -basis to the standard basis by applying the V -matrix to x , and go from the standard basis to the V -basis by applying V^{-1} .

Change of Basis Diagram

- When you are doing change of basis for systems of equations, it is useful to use a diagram mapping transformations between basis
- Given T , to find T_a you would trace the path from u_a to v_a , applying each transformation to the left of the previous:


$$A \implies TA \implies A^{-1}TA$$

$$T_a = A^{-1}TA$$

- Step by step, we have

$$Au_a = u \implies TAu_a = v \implies$$

$$A^{-1}TAu_a = v_a$$

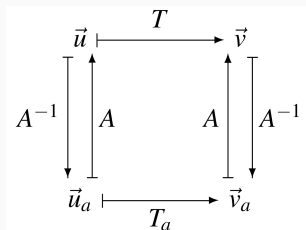

Diagonalization

Diagonalization

- The idea is that we want to change into a basis in which the system $A\vec{x} = \vec{y}$ is represented by a diagonal matrix. So how do we find such basis?
- Remember that for all eigenvalue-eigenvector pairs we have:
 $A\vec{v} = \lambda\vec{v}$
- Let's use our eigenvectors as our basis. Doing so we obtain:

$$\vec{x} = V\tilde{\vec{x}}, \vec{y} = V\tilde{\vec{y}}, \text{ and } \Lambda\tilde{\vec{x}} = \tilde{\vec{y}}$$

Where the upper-case lambda represents the diagonal matrix with eigenvalues on the diagonals.

- Transforming back to the standard basis, we get:

$$A = V\Lambda V^{-1}$$

Diagonalization Cont.

- Let's analyze this a bit further, why is it important to be able to do this?
- We see that diagonalizing the matrix makes the system much easier to solve, why?
- Also, we see that there is a “home state” for every system of linearly independent equations, i.e. the space in which the system's components are uncoupled.

2 Minute Break!

Differential Equations

Solving Differential Equations

Differentiation is linear!

$$\frac{d(c_1x(t) + c_2y(t))}{dt} = c_1 \frac{dx(t)}{dt} + c_2 \frac{dy(t)}{dt}$$

Solving systems of differential equations

Write the system in the following form:

$$\frac{dx(t)}{dt} = Ax(t)$$

Find the eigenvalues/eigenvectors of A and transform the system into the eigenbasis. If A has distinct eigenvalues, the general solution is:

$$x(t) = c_1 e^{\lambda_1 t} \vec{v}_1 + c_2 e^{\lambda_2 t} \vec{v}_2$$

Then, change back to the standard basis.

Example: second-order differential equations

Solve the following differential equation:

$$\ddot{x} - \dot{x} - 2x = 0$$

$$x(0) = 2, \dot{x}(0) = 1$$

Example: second-order differential equations

$$\ddot{x} - \dot{x} - 2x = 0, x(0) = 2, \dot{x}(0) = 1$$

Solution:

Write in matrix form and find eigenvectors:

$$\begin{bmatrix} \dot{x} \\ \ddot{x} \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ 2 & 1 \end{bmatrix} \begin{bmatrix} x \\ \dot{x} \end{bmatrix}$$

$$\lambda_1 = 2, v_1 = \begin{bmatrix} 1 \\ 2 \end{bmatrix}, \lambda_2 = -1, v_2 = \begin{bmatrix} -1 \\ 1 \end{bmatrix}$$

Use general form to solve:

$$\begin{bmatrix} x \\ \dot{x} \end{bmatrix} = c_1 e^{2t} v_1 + c_2 e^{-t} v_2$$

Example: second-order differential equations

$$\ddot{x} - \dot{x} - 2x = 0, x(0) = 2, \dot{x}(0) = 1$$

Solution:

Now plug in initial conditions:

$$\begin{bmatrix} 2 \\ 1 \end{bmatrix} = \begin{bmatrix} x(0) \\ \dot{x}(0) \end{bmatrix} = c_1 v_1 + c_2 v_2 = \begin{bmatrix} c_1 - c_2 \\ 2c_1 + c_2 \end{bmatrix}$$

Solving, we get $c_1 = 1, c_2 = -1$

$$\text{so } x(t) = e^{2t} + e^{-t}$$

Example: second-order differential equations

$$\ddot{x} - \dot{x} - 2x = 0, x(0) = 2, \dot{x}(0) = 1$$


Solution:

Sanity check: compute derivatives and check that the original system is satisfied

$$x(t) = e^{2t} + e^{-t}, \dot{x}(t) = 2e^{2t} - e^{-t}, \ddot{x}(t) = 4e^{2t} + e^{-t}$$

$$\implies \ddot{x} - \dot{x} - 2x = 0, x(0) = 2, \dot{x}(0) = 1$$

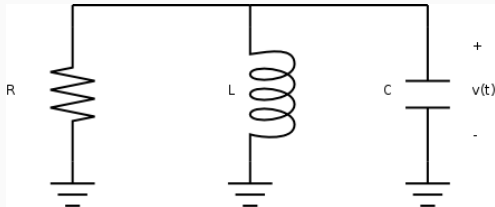Example: second-order differential equations



Given $x(t) = \begin{bmatrix} v(t) \\ i_L(t) \end{bmatrix}$

find matrix A such that $\frac{dx}{dt} = Ax$

Example: second-order differential equations

Direct all currents into ground.


$$i_R + i_L + i_C = 0$$

$$\frac{V}{R} + i_L = -C \frac{dV}{dt}$$

$$-\frac{1}{CR} V + -\frac{1}{C} i_L = \frac{dV}{dt}$$


Also
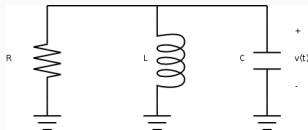
$$L \frac{di_L}{dt} = V \implies A = \begin{bmatrix} -\frac{1}{RC} & -\frac{1}{C} \\ \frac{1}{L} & 0 \end{bmatrix}$$



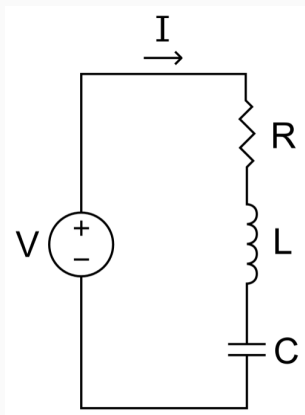Example: second-order differential equations

At $t < 0$, the circuit is at steady state.
At $t \geq 0$, the voltage source is set to 0. Find a differential equation for i_L for $t \geq 0$.




Example: second-order differential equations

Solution: use KCL/KVL to get

$$i_R = i_L = i_C, V_C + V_R + V_L = 0$$

$$\frac{V_R}{R} = i_L = C \frac{dV_C}{dt}, \frac{1}{C} i_L + R \frac{di_L}{dt} + L \frac{d^2 i_L}{dt^2} = 0$$
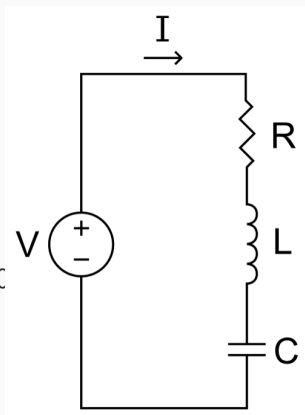
$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{d^2 i_L}{dt^2} \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} i_L \\ \frac{di_L}{dt} \end{bmatrix}$$



Example: second-order differential equations

If $R = 0$, $L = C = 1$, solve the differential equation:

Initial conditions: $i_L(0) = 0$,


$$\frac{di_L}{dt}(0) = -V_c = -V$$

Differential equation:

$$\begin{bmatrix} \frac{di_L}{dt} \\ \frac{d^2 i_L}{dt^2} \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\frac{1}{LC} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} i_L \\ \frac{di_L}{dt} \end{bmatrix}$$

$$\lambda_1 = i, v_1 = \begin{bmatrix} i \\ -1 \end{bmatrix}$$
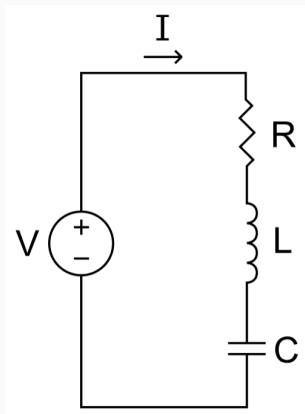
$$\lambda_2 = -i, v_2 = \begin{bmatrix} i \\ 1 \end{bmatrix}$$



Example: second-order differential equations


$$\begin{bmatrix} i_L \\ \frac{di_L}{dt} \end{bmatrix} = c_1 e^{it} v_1 + c_2 e^{-it} v_2$$

$$ic_1 + ic_2 = 0, -c_1 + c_2 = -V$$

$$\Rightarrow c_1 = \frac{V}{2}, c_2 = -\frac{V}{2}$$


so
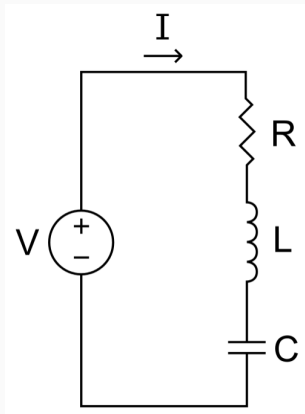
$$i_L = \frac{V}{2} i e^{it} - \frac{V}{2} e^{-it}$$



What do we do with different types of eigenvalues?

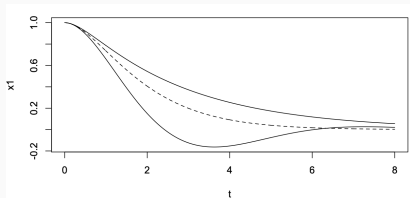Each interesting “case” of eigenvalues (real, imaginary, and repeated) is complementary to a case of resonance in 2d ODEs, so let's discuss them together:



Overdamping: two real eigenvalues


- When a system has two real eigenvalues, it will have two real eigenvectors, so the solution will be a combination of exponentials in the form

$$ae^{\lambda_1 t} + be^{\lambda_2 t}$$

- For negative lambdas, this produces exponential decay.

At large t , greater eigenvalue dominates behavior, so how fast the system approaches to 0 is determined by the larger eigenvalue.

■

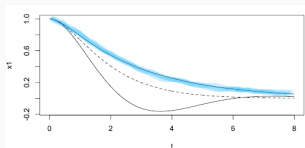

Underdamping: imaginary or complex eigenvalues


- You can still solve the system of differential equations as usual, but your solutions will be complex:

$$(a_1j + b_1)e^{c_1j+d_1} + (a_2j + b_2)e^{c_2j+d_2}$$

- You can rearrange terms and apply Euler's formula to write each term as a real exponential multiplied by a sinusoid

$$e^{d_1}(\alpha_1 \sin(\dots) + \beta_1 \cos(\dots)) + e^{d_2}(\alpha_2 \sin(\dots) + \beta_2 \cos(\dots))$$

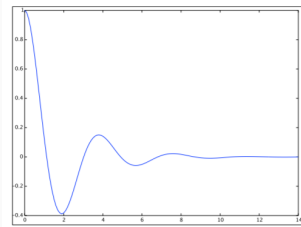If d_1 and d_2 are negative, then you can think of this as a sinusoid where the amplitude decays to 0



■

Critical Damping: repeated eigenvalue


- You only get one linearly independent eigenvector.
- So, arbitrarily choose the second column of your V matrix (making sure it is linearly independent from the eigenvector v_1)
- Compute A_v using the change of basis diagram $A_v = V^{-1}AV$
- This gives you an upper-triangular matrix
- The bottom row of the matrix gives you an equation in one variable (only depends on the second component of x_v), which you can solve to get something in the form of $x_{v,2} = ae^{\lambda t}$

Critical Damping: repeated eigenvalue

- The top row of the matrix depends on both components of x_v , but you can plug in the value you got for $x_{v,2}$ and then solve for $x_{v,1}$
- If you solve this differential equation (which is a diff eq with a non-constant input*), you'll get an equation in the form:

$$x(t) = c_1 e^{-\lambda t} + c_2 t e^{-\lambda t}$$

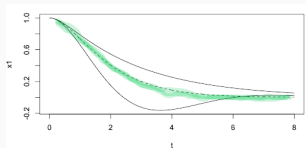The critically damped case gives us the fastest-decaying exponential that doesn't oscillate



*You can solve this using the formula

$$x_p(t) = x_0 e^{\lambda t} + \int_0^t u(\tau) e^{\lambda(t-\tau)} d\tau$$

2 Minute Break!

Phasors

- Phasors express the response of a circuit to a sinusoidal input
- Any real, periodic signal can be expressed as the sum of sinusoids - we can apply this technique very broadly!
- A phasor encodes information about amplitude and phase, but not frequency

$$v_s = A \cos(\omega t + \phi) \rightarrow \tilde{V}_s = \frac{A}{2} e^{j\phi}$$

Impedance

- Impedance (Z) is a generalized form of resistance - expresses a component's response to an alternating current
- Each common passive circuit element (resistor, capacitor, and inductor) has a characteristic impedance

$$Z_R = R$$


$$Z_C = \frac{1}{j\omega C}$$

$$Z_L = j\omega L$$

Phasor Analysis Procedure


1. Express all time domain signals as cosines
2. Convert voltages, currents, and impedances to their phasor equivalents
3. Set up phasor equations and solve for unknowns
4. Transform back to time domain

Phasor Practice

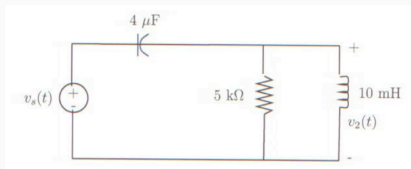

Let $v_s(t) = 5 \cos(5000t + \frac{\pi}{4})$. Find $v_2(t)$.


Phasor Practice

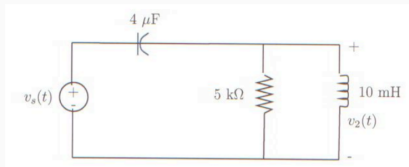

1. Translate to phasor domain

- $\omega = 5000$
- $v_s(t) = 5 \cos(5000t + \frac{\pi}{4}) \rightarrow \tilde{V}_s = \frac{5}{2} e^{j\frac{\pi}{4}}$
- $C = 4\mu\text{F} \rightarrow Z_C = \frac{1}{j(4 \cdot 10^{-6})(5000)} = -j50$
- $R = 5\text{k}\Omega \rightarrow Z_R = 5 \cdot 10^3$
- $L = 10\text{mH} \rightarrow Z_L = j(5000)(10 \cdot 10^{-3}) = j50$

Phasor Practice

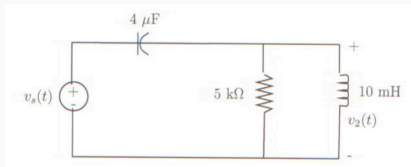


2. Solve for \tilde{V}_2

- Set up as impedance divider:

$$\frac{\tilde{V}_s}{Z_C + (Z_R \parallel Z_L)} = \frac{\tilde{V}_2}{Z_R \parallel Z_L}$$

$$\tilde{V}_2 = \tilde{V}_s \frac{Z_R \parallel Z_L}{Z_C + (Z_R \parallel Z_L)} = \tilde{V}_s \frac{\frac{Z_R Z_L}{Z_R + Z_L}}{\frac{Z_R Z_L + Z_R Z_C + Z_L Z_C}{Z_R + Z_L}}$$

Phasor Practice

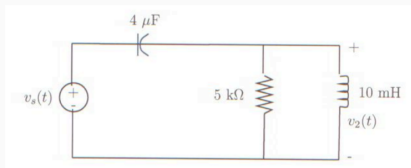


2. Solve for \tilde{V}_2

$$\tilde{V}_2 = \tilde{V}_s \frac{Z_R Z_L}{Z_R Z_L + Z_R Z_C + Z_L Z_C} = \tilde{V}_s \frac{j2.5 * 10^5}{j2.5 * 10^5 - j2.5 * 10^5 + 2500}$$

$$\tilde{V}_2 = j100 \tilde{V}_s = 100 \tilde{V}_s e^{j\frac{\pi}{2}}$$

Phasor Practice

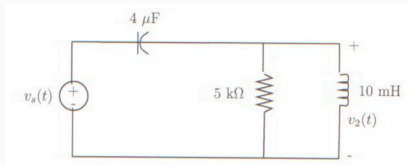

3. Find time-domain solution


- $\tilde{V}_2 = 100e^{j\frac{\pi}{2}} \tilde{V}_s \rightarrow v_2(t) = 100v_s(t + \frac{\pi}{2}) = 500 \cos(5000t + \frac{3\pi}{4})$

Transfer Function Review

A ***transfer function*** of a circuit or system describes the **output response** to an **input excitation** as a function of the angular frequency ω .

$$H(\omega) = \frac{V_{out}(\omega)}{V_{in}(\omega)}$$


RC Circuits

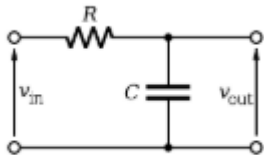

$$H(\omega) = \frac{1}{1+j\omega RC}$$

Low pass:
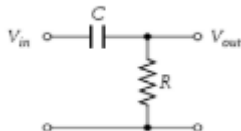
$$\lim_{\omega \rightarrow \infty} H(\omega) = 0, H(0) = 1$$



$$H(\omega) = \frac{j\omega RC}{1+j\omega RC}$$

High pass:

$$\lim_{\omega \rightarrow \infty} H(\omega) = 1, H(0) = 0$$

Bode Plot Review

$$V[dB] = 20 \log_{10}\left(\frac{V}{V_0}\right)$$





- Bode plots provide a way for us to easily visualize the output response of our system, depending on the input frequency ω .
- Because Bode plots are in log scale for ω , we are able to take advantage of the properties of logs.
 - $G = XY \implies G[dB] = X[dB] + Y[dB]$
 - $G = \frac{X}{Y} \implies G[dB] = X[dB] - Y[dB]$

Hence, we can break our transfer function $H(\omega)$ into a product of familiar transfer functions (simple poles, quadratic zeros, etc. - “functional forms”), graph them out individually, and then add them together on the graph.

Bode Plot Review

- We want to be able to plot the transfer function as a function of the frequency ω .
- However, it's a complex valued function so it's easier to have a plot for the magnitude and one for the phase.
- Because the magnitude plot is in log scale, and the phase plot is in semi-log scale we are able to take advantage of the properties of logs.
 - $\log(XY) = \log(X) + \log(Y)$
- Hence, we can break our transfer function $H(\omega)$ into a product of familiar transfer functions (simple poles, quadratic zeros, etc. - “functional forms”), graph them out individually, and then add them together on the graph.


RC Circuits, revisited

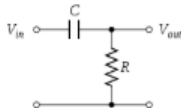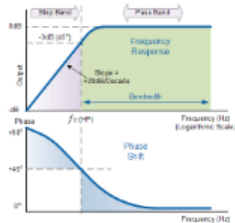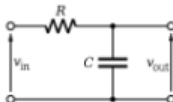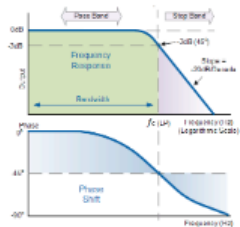

$$H(\omega) = \frac{1}{1+j\omega RC}$$

$$H(\omega) = \frac{j\omega RC}{1+j\omega RC}$$

Common Filters and their Bode Plots

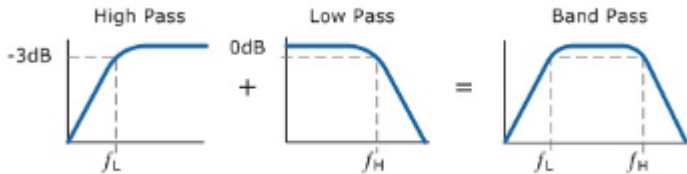


In the high pass filter, the frequencies greater than the corner frequency have a gain of 0dB (so they aren't changed), while frequencies less than the corner frequency have a gain $< 0\text{dB}$ (so they are multiplied by something less than 1).

In the lowpass filter, the opposite is true.

State-Space Representations


State Space Modeling: Example

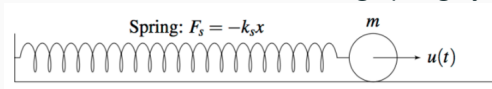Assume we have the following spring system:



State Space Modeling: Example

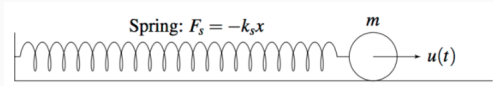Assume we have the following spring system:



We can model the system as a linear continuous time state space model:


$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

$$\vec{y}(t) = C\vec{x}(t)$$

in which:

$$\vec{x}(t) = \begin{bmatrix} x(t) \\ v(t) \end{bmatrix}, A = \begin{bmatrix} 0 & 1 \\ -\frac{k_s}{m} & 0 \end{bmatrix}, \vec{b} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}, \text{ and } C = \begin{bmatrix} 0 & 1 \end{bmatrix}$$

State Space Modeling:

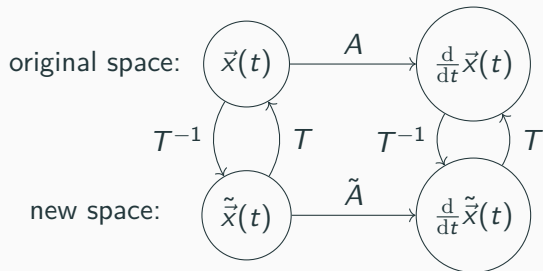

Always apply operations to right side first

$$\tilde{A} = T^{-1}AT$$

$$\tilde{\vec{x}}(t) = T^{-1}\vec{x}(t)$$

State Space Modeling Procedure:

1. Set up differential equation of the form:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

State Space Modeling Procedure:

1. Set up differential equation of the form:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

2. Find λ_i of A ; let $\tilde{A} = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & 0 & \vdots \\ \vdots & 0 & \ddots & 0 \\ 0 & \cdots & 0 & \lambda_n \end{bmatrix}$

State Space Modeling Procedure:

1. Set up differential equation of the form:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

2. Find λ_i of A ; let $\tilde{A} = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & 0 & \vdots \\ \vdots & 0 & \ddots & 0 \\ 0 & \cdots & 0 & \lambda_n \end{bmatrix}$

3. Find eigenvectors \vec{v}_i of A ; let $T = \begin{bmatrix} \vec{v}_1 & \vec{v}_2 & \cdots & \vec{v}_n \end{bmatrix}$

State Space Modeling Procedure:

1. Set up differential equation of the form:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

2. Find λ_i of A ; let $\tilde{A} = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & 0 & \vdots \\ \vdots & 0 & \ddots & 0 \\ 0 & \cdots & 0 & \lambda_n \end{bmatrix}$

3. Find eigenvectors \vec{v}_i of A ; let $T = \begin{bmatrix} \vec{v}_1 & \vec{v}_2 & \cdots & \vec{v}_n \end{bmatrix}$

4. Convert $\vec{x}(t)$ to $\tilde{\vec{x}}(t)$ using: $\tilde{\vec{x}}(t) = T^{-1}\vec{x}(t)$

State Space Modeling Procedure:

1. Set up differential equation of the form:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

2. Find λ_i of A ; let $\tilde{A} = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & 0 & \vdots \\ \vdots & 0 & \ddots & 0 \\ 0 & \cdots & 0 & \lambda_n \end{bmatrix}$

3. Find eigenvectors \vec{v}_i of A ; let $T = \begin{bmatrix} \vec{v}_1 & \vec{v}_2 & \cdots & \vec{v}_n \end{bmatrix}$

4. Convert $\vec{x}(t)$ to $\tilde{\vec{x}}(t)$ using: $\tilde{\vec{x}}(t) = T^{-1}\vec{x}(t)$

5. Solve $\frac{d}{dt}\tilde{\vec{x}}(t) = \tilde{A}\tilde{\vec{x}}(t) + T\vec{b}u(t)$

State Space Modeling Procedure:

1. Set up differential equation of the form:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + \vec{b}u(t)$$

2. Find λ_i of A ; let $\tilde{A} = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & 0 & \vdots \\ \vdots & 0 & \ddots & 0 \\ 0 & \cdots & 0 & \lambda_n \end{bmatrix}$

3. Find eigenvectors \vec{v}_i of A ; let $T = \begin{bmatrix} \vec{v}_1 & \vec{v}_2 & \cdots & \vec{v}_n \end{bmatrix}$

4. Convert $\vec{x}(t)$ to $\tilde{\vec{x}}(t)$ using: $\tilde{\vec{x}}(t) = T^{-1}\vec{x}(t)$

5. Solve $\frac{d}{dt}\tilde{\vec{x}}(t) = \tilde{A}\tilde{\vec{x}}(t) + T\vec{b}u(t)$

6. Convert solution back to $\vec{x}(t)$

State Space Modeling:

Continuous time solution:

$$\tilde{x}(t) = e^{\lambda t} \tilde{x}(0) + \frac{e^{\lambda t} - 1}{\lambda} u(t) + w(t)$$

Discrete time solution:

$$x_d(i+1) = e^{\lambda \Delta} x_d(i) + \frac{e^{\lambda \Delta} - 1}{\lambda} u(i) + w(i)$$

Stability, Observability, and Controllability

given:

$$\vec{x}(i+1) = A\vec{x}(i) + Bu(i)$$

$$\vec{y}(i) = C\vec{x}(i)$$

in which:

\vec{x} is our state,

\vec{u} is our input,

\vec{y} is what we can observe:

Stability (Discrete time):

Discrete time model:

if $|\lambda_i| < 1$ for all λ_i of A , system is stable

intuition: if any $|\lambda_i| \geq 1$, state vector is increasing each time step
will be infinitely magnified over time

Stability (Continuous time):

Continuous time model:

if the $\Re\{\lambda_i\} < 0$ for all λ_i of A are strictly negative, system is stable

intuition: if real part of eigenvalue is positive, state vector is increasing over time and will be infinitely magnified over time

Feedback:

if system is controllable, we can set: $u(t) = K\vec{x}(t)$

plugging in, we get: $\vec{x}(t+1) = (A + BK)\vec{x}(t)$

we can find the eigenvalues of $(A + BK)$ to check for stability

Stability Example:

given the following system:

$$\vec{x}[t+1] = \begin{bmatrix} -5 & 0 \\ 7 & 6 \end{bmatrix} \vec{x}[t] + \begin{bmatrix} 2 \\ -1 \end{bmatrix} u[t]$$

$$\vec{y}[t] = \begin{bmatrix} 1 & 1 \end{bmatrix} \vec{x}[t]$$

Stability Check:

$$\lambda = 6, -5$$

Stability Check:

$$\lambda = 6, -5$$

System is unstable

Thanks for coming!

hkn.mu/feedback